



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade (3rd Cycle)
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

16EC302 – TRANSMISSION LINES AND ANTENNAS


III YEAR/ V SEMESTER

UNIT 1 – TRANSMISSION LINE THEORY

TOPIC 5 – INPUT & TRANSFER IMPEDANCE



INPUT IMPEDANCE OF A LINE

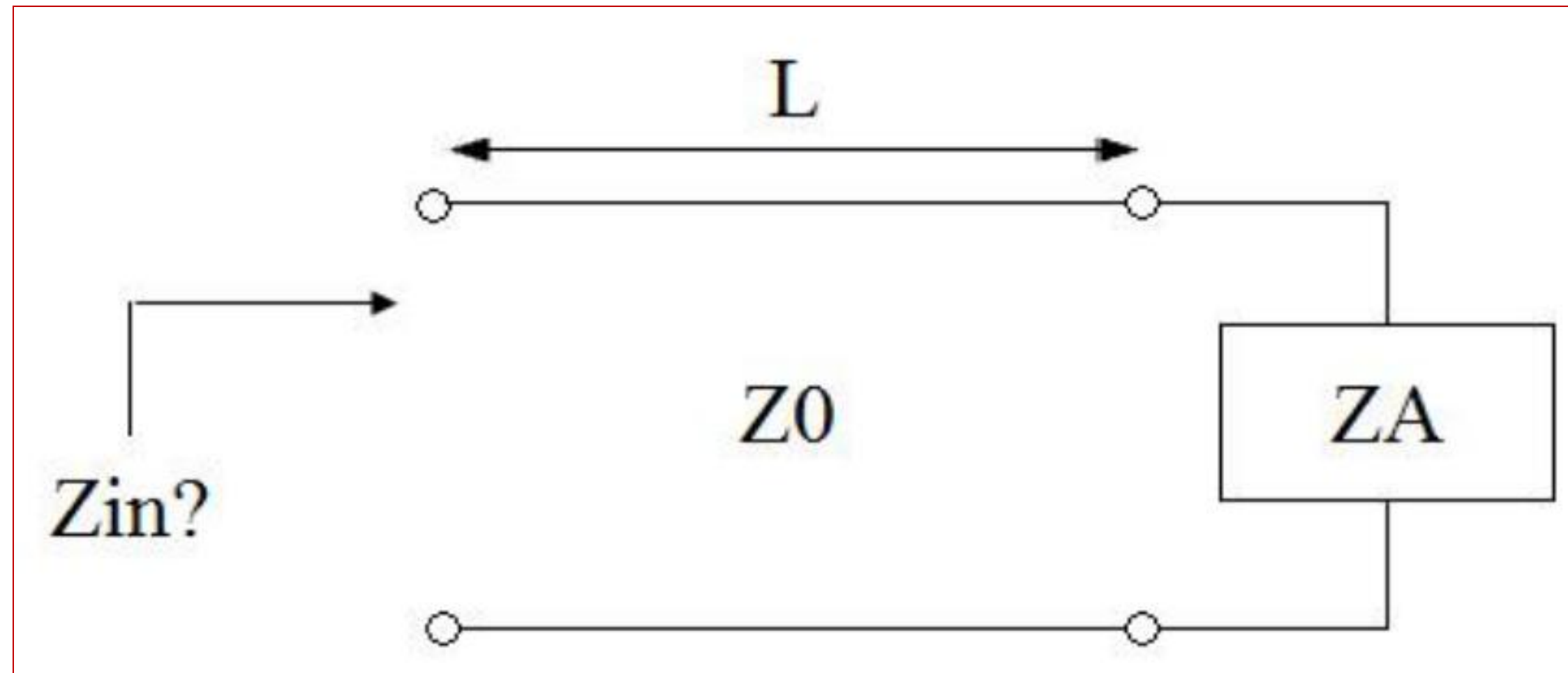

What is Z_{in} or Input impedance of a transmission line?




INPUT IMEDANCE OF A LINE

- Input impedance of a transmission line is defined as the impedance measured across the input terminals of the transmission lines
- It is the impedance seen looking into the sending end or the input terminals
- It is also the impedance at the input into which the source must work when the line is connected



INPUT IMPEDANCE OF A LINE

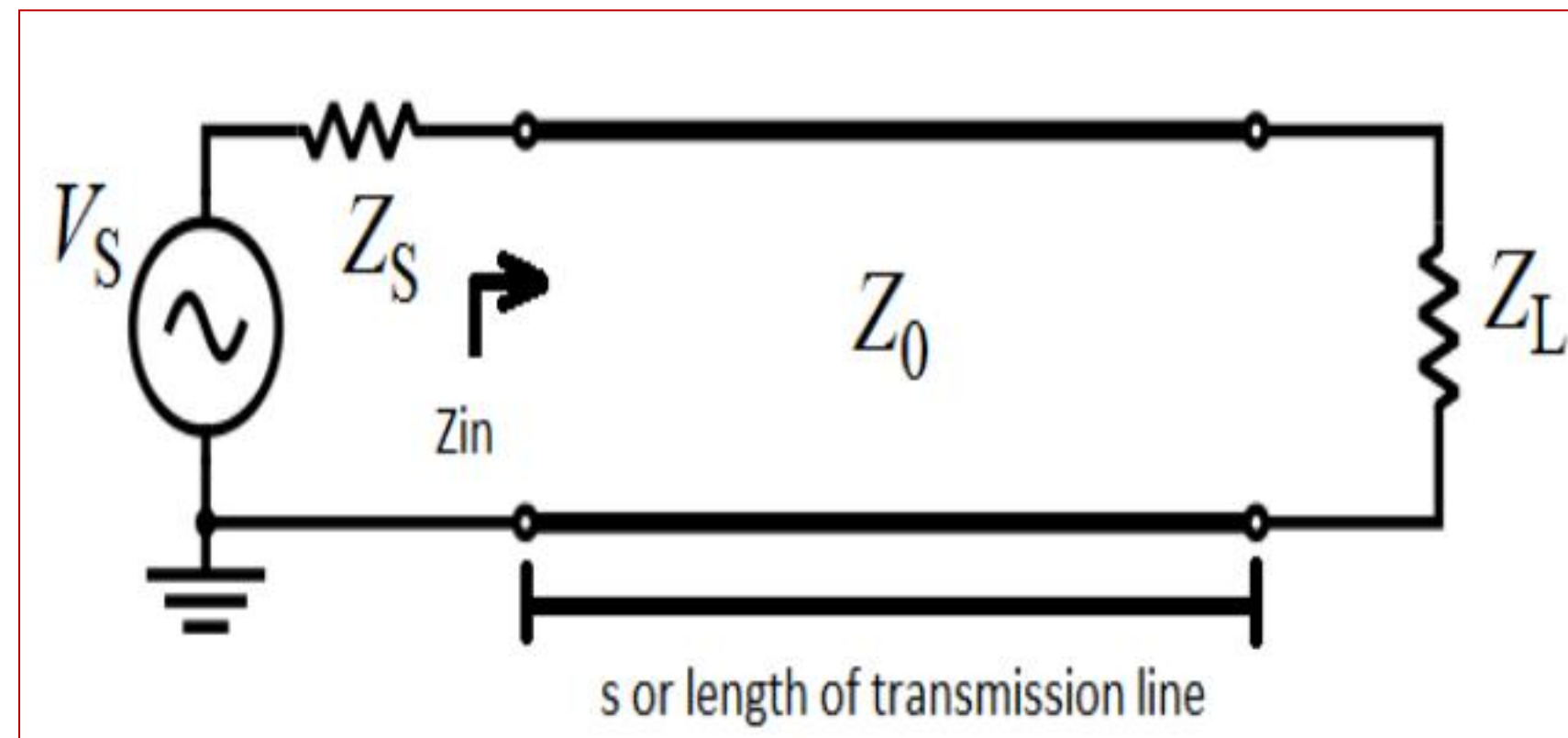- Also known as driving point impedance
- Denoted by $Z_{in} = V_s/I_s$
- Also known as driving point impedance





INPUT IMEDANCE OF A LINE – STANDARD FORMS



• FIRST FORM

The voltage and current expressions – Hyperbolic form

$$E = E_R \cosh \sqrt{zy} s + I_R Z_0 \sinh \sqrt{zy} s \quad \text{----- (1)}$$

$$I = I_R \cosh \sqrt{zy} s + \frac{E_R}{Z_0} \sinh \sqrt{zy} s \quad \text{----- (2)}$$

To find input voltage & input current for the transmission line of length l , replace s by l , \sqrt{zy} by γ , E by E_s & I by I_s in equations (1) & (2),

$$E_s = E_R \cosh \gamma l + I_R Z_0 \sinh \gamma l \quad \text{----- (3)}$$

$$I_s = I_R \cosh \gamma l + \frac{E_R}{Z_0} \sinh \gamma l \quad \text{----- (4)}$$



INPUT IMPEDANCE OF A LINE



Input Impedance $Z_s = E_s / I_s$

Therefore, Eqn (3) / Eqn (4) gives,

$$E_s = I_R Z_R \cosh \gamma l + I_R Z_0 \sinh \gamma l$$

$$I_s = I_R \cosh \gamma l + \frac{I_R Z_R}{Z_0} \sinh \gamma l$$

$$Z_s = Z_0 \left[\frac{Z_R \cosh \gamma l + Z_0 \sinh \gamma l}{Z_0 \cosh \gamma l + Z_R \sinh \gamma l} \right] \quad \text{----- (5)}$$

Equation (5) is one of the standard form of input impedance of a transmission line.



INPUT IMEDADANCE OF A LINE



- **SECOND FORM**

$$E = \frac{E_R (Z_R + Z_0)}{2Z_R} \left[\frac{e^{\sqrt{zy} s} + \frac{(Z_R - Z_0)}{(Z_R + Z_0)} e^{-\sqrt{zy} s}}{(Z_R + Z_0)} \right] \text{----- (6)}$$

$$I = \frac{I_R (Z_R + Z_0)}{2Z_R} \left[\frac{e^{\sqrt{zy} s} - \frac{(Z_R - Z_0)}{(Z_R + Z_0)} e^{-\sqrt{zy} s}}{(Z_R + Z_0)} \right] \text{----- (7)}$$

To find input voltage & input current for the transmission line of length l , replace s by l , \sqrt{zy} by γ , E by E_s & I by I_s in equations (1) & (2) & by getting E_s / I_s



INPUT IMEDANCE OF A LINE

- **SECOND FORM**

$$E = \cancel{I_R} \cancel{Z_R} (Z_R + Z_0) \left[\frac{e^{\gamma l} + (Z_R - Z_0) e^{-\gamma l}}{(Z_R + Z_0)} \right] \text{----- (6)}$$

$$I = \cancel{I_R} (Z_R + Z_0) \left[\frac{e^{\gamma l} - (Z_R - Z_0) e^{-\gamma l}}{(Z_R + Z_0)} \right] \text{----- (7)}$$

$$Z_s = Z_0 \left[\frac{e^{\gamma l} + (Z_R - Z_0) e^{-\gamma l}}{(Z_R + Z_0)} \right] \text{----- (8)}$$
$$\left[\frac{e^{\gamma l} - (Z_R - Z_0) e^{-\gamma l}}{(Z_R + Z_0)} \right]$$

Eqn (8) is the another form of input impedance of a transmission line



INPUT IMPEDANCE OF A LINE



Input impedance is given by

$$Z_{\text{in}}(\ell) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma \ell)}{Z_0 + Z_L \tanh(\gamma \ell)}$$

$$\tanh(j\theta) = j \tan \theta$$

$$\text{Subs } \gamma = j\beta, Z_0 \tanh \gamma l = j Z_0 \tan \beta l$$



INPUT IMPEDANCE OF A LOSSLESS LINE



- For a lossless transmission line, Input impedance is purely imaginary and is given by $\gamma = j \beta$
- Therefore the input impedance is given by,

$$Z_{\text{in}}(\ell) = Z_0 \frac{Z_L + j Z_0 \tan(\beta \ell)}{Z_0 + j Z_L \tan(\beta \ell)}$$

where $\beta = \frac{2\pi}{\lambda}$ is the wavenumber.



INPUT IMPEDANCE OF SPECIAL CASES OF LINE



➤ Matched load

Another special case is when the load impedance is equal to the characteristic impedance of the line (i.e. the line is matched), in which case the impedance reduces to the characteristic impedance of the line so that,

$$Z_{in} = Z_0 = Z_L$$






INPUT IMPEDANCE OF SPECIAL CASES OF LINE



➤ Short line

For the case of a shorted load (i.e $Z_L = 0$), the input impedance is purely imaginary and a periodic function of position and wavelength (frequency)

$$Z_{in}(l) = j Z_0 \tan(\beta l)$$

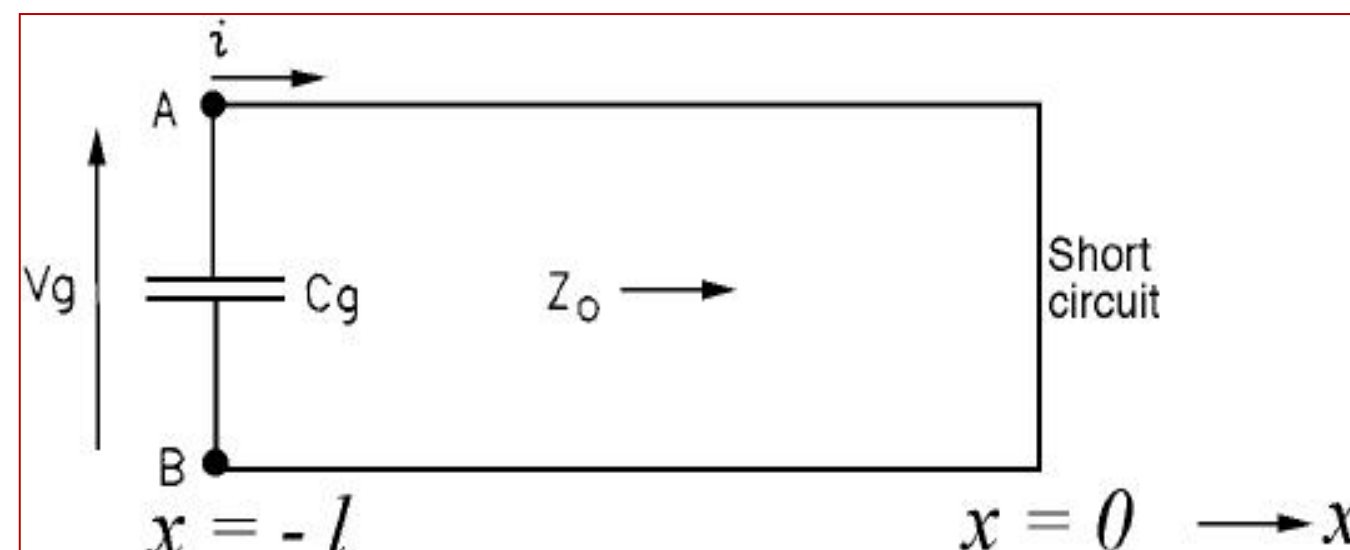




INFINITE LINE



- When the length l of the line is infinite, i.e l approaches to infinity, thus

$$Z_{in} = Z_0$$

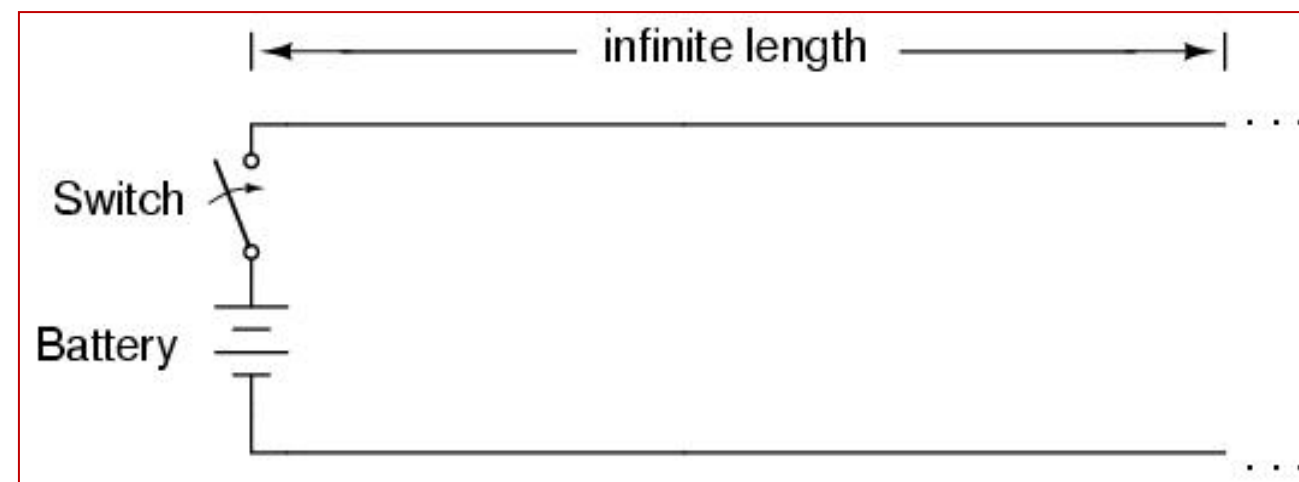- Hence it is concluded that a line of infinite length irrespective of the type of terminating load, has an input impedance Z_0 , thus behaving like a line of finite length terminated in its characteristic impedance Z_0





TRANSFER IMPEDANCE



- Input voltage of a transmission line is

$$E_s = \frac{E_R (Z_R + Z_0)}{2Z_R} \left[\frac{e^{\sqrt{zy}s} + \frac{(Z_R - Z_0)}{(Z_R + Z_0)} e^{-\sqrt{zy}s}}{(Z_R + Z_0)} \right]$$

Subs E_R by $I_R Z_R$ in the above expression, we get

$$E_s = \frac{I_R Z_R (Z_R + Z_0)}{2Z_R} \left[\frac{e^{\sqrt{zy}s} + \frac{(Z_R - Z_0)}{(Z_R + Z_0)} e^{-\sqrt{zy}s}}{(Z_R + Z_0)} \right]$$

Subs. Reflection co-efficient $k = (Z_R - Z_0) / (Z_R + Z_0)$



TRANSFER IMPEDANCE



➤ Transfer Impedance $Z_T = E_s / I_R$

$$\frac{Z_T = E_s}{I_R} = \frac{(Z_R + Z_0)}{2} e^{\sqrt{zy} s} + \frac{(Z_R - Z_0)}{2} e^{-\sqrt{zy} s}$$

Rearranging the above expression, we get,

$$Z_T = \frac{Z_R}{2} e^{\sqrt{zy} s} + \frac{Z_R}{2} e^{-\sqrt{zy} s} + \frac{Z_0}{2} e^{\sqrt{zy} s} - \frac{Z_0}{2} e^{-\sqrt{zy} s}$$
$$Z_T = Z_R \cosh \sqrt{zy} s + Z_0 \sinh \sqrt{zy} s$$



ASSESSMENT



1. Define input impedance of a transmission line.
2. Give the standard form of input impedance of a lossless line.
3. What is infinite line.
4. Compare the input impedances of half wave and quarter wave lines.
5. What is Transfer Impedance?



THANK YOU