 




Topic 1.8 : FET- Self Bias configuration

3. Self Bias



- * The gate-source junction is always reverse biased.
- * The condition requires negative V_{GS} for n-channel JFET & a positive V_{GS} for p-channel JFET.
- * The R_G does not affect the bias because it has essentially no voltage drop across it.
- * \therefore The Gate remains at 0V.
- * The voltage drop across resistor R_S makes the gate-source junction reverse biased.

* I_S produces voltage drop across R_S & makes the source positive w.r.t. ground.

Since

$$I_S = I_D \text{ \& } V_G = 0 \text{ Then } V_S = I_S R_S = I_D R_S$$

* The Gate-Source Voltage is

$$V_{GS} = V_G - V_S = 0 - I_D R_S = -I_D R_S$$

For p channel:

* The voltage drop across R_S & makes the source negative w.r.t. ground.

Since


$$I_S = I_D \text{ \& } V_G = 0 \text{ Then } V_S = -I_S R_S = -I_D R_S$$

* The Gate-Source Voltage is

$$V_{GS} = V_G - V_S = 0 - (-I_D R_S) = I_D R_S$$

DC Analysis:

For n-channel

 

For dc analysis the coupling capacitors are replaced by open circuit & R_G is replaced by short circuit equivalent, since $I_G = 0$.

W.K.T

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad \text{--- (1)}$$

(18)



Substitute the value of V_{GS} in eqn ①

$$\text{①} \Rightarrow I_D = I_{DSS} \left(1 - \frac{(-I_D R_S)}{V_P} \right)^2 \rightarrow \text{for n-channel}$$

$$= I_{DSS} \left(1 + \frac{I_D R_S}{V_P} \right)^2$$

Apply KVL to the Drain to source junction

$$V_S + V_{DS} + I_D R_D - V_{DD} = 0$$

$$\therefore V_{DS} = V_{DD} - V_S - I_D R_D$$

$$= V_{DD} - \underbrace{I_D R_S}_{V_S} - I_D R_D$$

$$\therefore V_{DS} = V_{DD} - I_D (R_S + R_D)$$