 




Topic 1.7 : Biasing the FET & Fixed Bias configuration

Design of biasing for JFET

* FET - Field Effect Transistor - It's a semiconductor device which depends for its operation on the control of current by an electric field.





FET differs from the BJT in the following characteristics

1. It's operation depends upon the flow of majority carriers only.
2. It's simpler to fabricate & occupies less space.
3. It exhibits a high input resistance, typically many megohms.
4. It's less noisy compared to BJT.
5. It exhibits no offset voltage at zero drain current.

Disadvantages of FET

- * Small gain bandwidth product.

Symbol:

  

* The general relationship that can be applied to the dc analysis of all FET amplifiers are


$$I_G = 0 \text{ Amps}$$

$$I_D = I_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$



1. Fixed Bias / Gate Bias

 

* To make the gate-source junction reverse biased a separate supply V_{GG} is connected such that gate is more negative than the source.


DC Analysis:

* For dc analysis coupling capacitors are open circuited.

* The current through R_G is I_G which is 0.

* This permits R_G to replace by short circuit

 equivalent, simplifying the fixed bias circuit.



* We know for dc analysis

$$I_G = 0 \text{ amps}$$

* Apply KVL to the gate to source junction

$$V_{GS} + V_{GG} = 0$$

$$\therefore V_{GS} = -V_{GG}$$

* Since V_{GG} is a fixed dc supply, the voltage V_{GS} is fixed in magnitude & hence the name fixed bias circuit

* For fixed bias circuit the I_D can be calculated as

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

* Apply KVL to the Drain to Source junction

$$V_{DS} + I_D R_D + V_{GS} = 0$$

$$\therefore V_{DS} = V_{DD} - I_D R_D$$

Q-Point

$$I_{DQ} = I_{DSS} \left[1 - \frac{V_{GSQ}}{V_p} \right]^2$$

$$V_{DSQ} = V_{DD} - I_{DQ} R_D$$