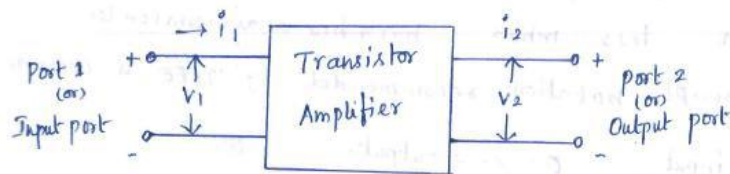




Topic 2.1 : Two port devices and Network parameters (Z,Y,H parameters)

Method of drawing Small-Signal Equivalent Circuit

- * A transistor can be treated as a two port Network.
- * The terminal behaviour of any 2 port network can be specified by the terminal voltage V_1 & V_2 at port 1 & port 2 respectively & currents i_1 & i_2 entering port 1 & 2 respectively as shown in Fig:



- * From 4 variables V_1, V_2 & i_1, i_2 2 can be selected as independent variables & remaining 2 can be expressed in terms of the independent variables.

- * The transistor can be analyzed using various 2 port parameters which of the following are more important.

1. Z - parameter (or) Impedance parameter
2. Y - parameter (or) Admittance parameter
3. H - parameter (or) Hybrid parameter.

H-parameter (or) Hybrid parameters: * 2Mark

- * If the input current i_1 & the output voltage V_2 are taken as independent variables, the input voltage V_1 & output current i_2 can be expressed as

$$V_1 = h_{11} i_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$i_2 = h_{21} i_1 + h_{22} V_2 \quad \text{--- (2)}$$

- * The 4 h-parameters $h_{11}, h_{12}, h_{21}, h_{22}$ are defined as

$$h_{11} = \left[\frac{V_1}{i_1} \right] \text{ with } V_2 = 0 \text{ in eqn (1)} \rightarrow \text{input impedance with output port short circuited.}$$



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

Approved by AICTE, New Delhi, Affiliated to Anna University, Chennai

Accredited by NAAC-UGC with 'A++' Grade (Cycle III) &

Accredited by NBA (B.E - CSE, EEE, ECE, Mech&B.Tech.IT)

COIMBATORE-641 035, TAMIL NADU



$h_{22} = \left[\frac{i_2}{v_2} \right]$ with $i_1 = 0$ in eqn ② \Rightarrow output admittance with input port short circuited.

$h_{12} = \left[\frac{v_1}{v_2} \right]$ with $i_1 = 0$ in eqn ① \Rightarrow Reverse voltage transfer gain with input port open circuited.

$h_{21} = \left[\frac{i_2}{i_1} \right]$ with $v_2 = 0$ in eqn ② \Rightarrow Forward current gain with output port short circuited.

* The dimensions of h-parameters are

$$h_{11} = \Omega \quad h_{22} = \text{mhos} \quad h_{21} \& h_{12} = \text{dimensionless}$$

* Alternate subscript notation recommended by IEEE is commonly used

$$i = 11 = \text{input}; \quad o = 22 = \text{output} \quad \text{--- ③}$$

$$f = 21 = \text{Forward Transfer}; \quad r = \text{reverse Transfer} \quad \text{--- ④}$$

* According to eqn ③ & ④ for common Emitter Amplifier


$$h_{11} = h_{ie}; \quad h_{22} = h_{oe} \quad \text{--- ⑤}$$

$$h_{12} = h_{re}; \quad h_{21} = h_{fe} \quad \text{--- ⑥}$$

$$\text{①} \Rightarrow v_1 = h_i i_1 + h_r v_2 \quad \text{--- ⑦}$$

$$\text{②} \Rightarrow i_2 = h_f i_1 + h_o v_2 \quad \text{--- ⑧}$$

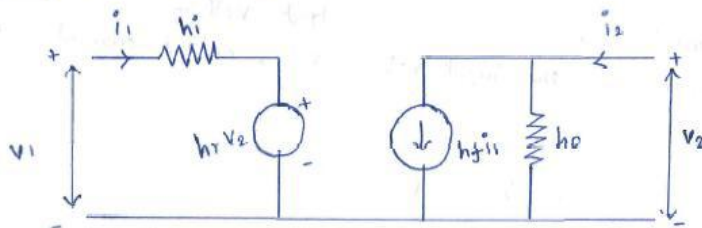* For this equation we want to draw equivalent circuit & verify using KVL to input, KCL to output node.



H-parameter for all the 3 configurations

Parameters	CE	CB	CC
Input resistance (h_{11})	h_{ie}	h_{ib}	h_{ic}
Reverse Voltage gain	h_{re}	h_{rb}	h_{rc}
Forward Transfer current gain	h_{fe}	h_{fb}	h_{fc}
Output admittance	h_{oe}	h_{ob}	h_{oc}



① Z parameters or Impedance parameters



i_1, i_2 - independent variables

V_1, V_2 - are given as

$$V_1 = Z_{11} i_1 + Z_{12} i_2$$

$$V_2 = Z_{21} i_1 + Z_{22} i_2$$

Four impedance parameters, Z_{11}, Z_{22}, Z_{12} and Z_{21} are defined as

$$Z_{11} = \left[\frac{V_1}{i_1} \right] \text{ with } i_2 = 0$$

= input impedance with output port open circuited

$$Z_{22} = \left[\frac{V_2}{i_2} \right] \text{ with } i_1 = 0$$

= output impedance with input port open circuited

$$Z_{12} = \left[\frac{V_1}{i_2} \right] \text{ with } i_1 = 0$$

= reverse transfer impedance with port 1 open circuited

$$Z_{21} = \left[\frac{V_2}{i_1} \right] \text{ with } i_2 = 0$$

= Forward transfer impedance with port 2 open circuited

② Y parameters or Admittance parameters

V_1, V_2 - independent variables

i_1, i_2 are given by

$$i_1 = Y_{11} V_1 + Y_{12} V_2$$

$$i_2 = Y_{21} V_1 + Y_{22} V_2$$

$Y_{11}, Y_{12}, Y_{21}, Y_{22}$ → short circuit admittance parameters
or simply admittance parameters



$$Y_{11} = \left[\frac{i_1}{v_1} \right] \text{ with } v_2 = 0$$

= input admittance with port 2 short circuited

$$Y_{22} = \left[\frac{i_2}{v_2} \right] \text{ with } v_1 = 0$$

= output admittance with port 1 short circuited

$$Y_{12} = \left[\frac{i_1}{v_2} \right] \text{ with } v_1 = 0$$

= reverse transfer admittance with port 1 short circuited

$$Y_{21} = \left[\frac{i_2}{v_1} \right] \text{ with } v_2 = 0$$

= Forward transfer admittance with port 2 short circuited