



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35

An Autonomous Institution

Accredited by NBA – AICTE and Accredited by NAAC – UGC with ‘A++’
Grade

Approved by AICTE, New Delhi & Affiliated to Anna University,
Chennai



DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB222- Digital Principles and Computer Organization

II AIML / III SEMESTER


UNIT 2 – Combinational Circuits

Encoder and Decoder



WHAT IS A DECODER?

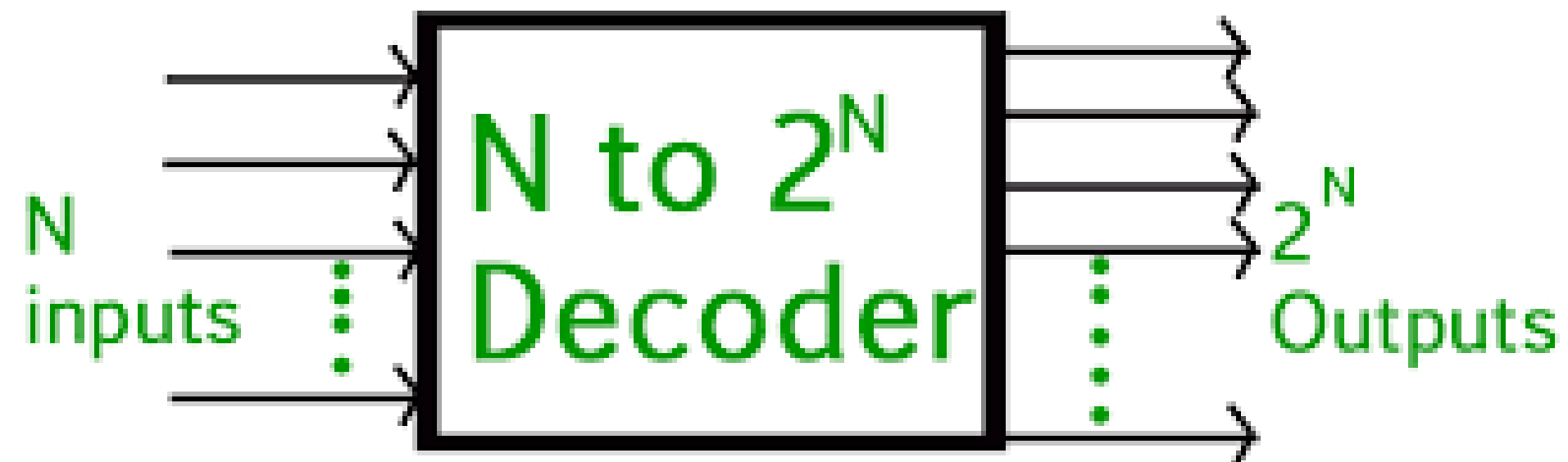- **Decoder** is a combinational logic circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs.





DECODER




A decoder has

- n inputs
 - 2^n outputs
- A decoder selects one of 2^n outputs by decoding the binary value on the n inputs.
 - The decoder generates all of the minterms of the n input variables.
- Exactly one output will be active for each combination of the inputs.

What does "active" mean?



DECODER

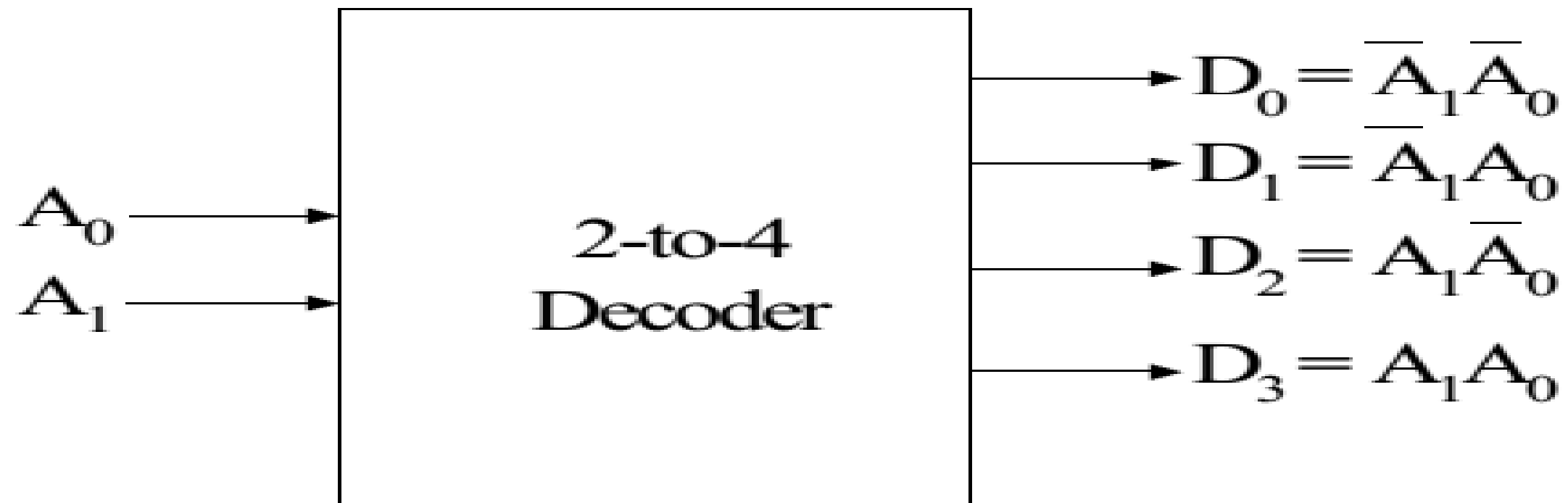

A 2-to-4 decoder without enable

Decimal #	Input		Output			
	A_1	A_0	D_0	D_1	D_2	D_3
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1


Truth table for 2-to-4 decoder



DECODER



Logic Diagram

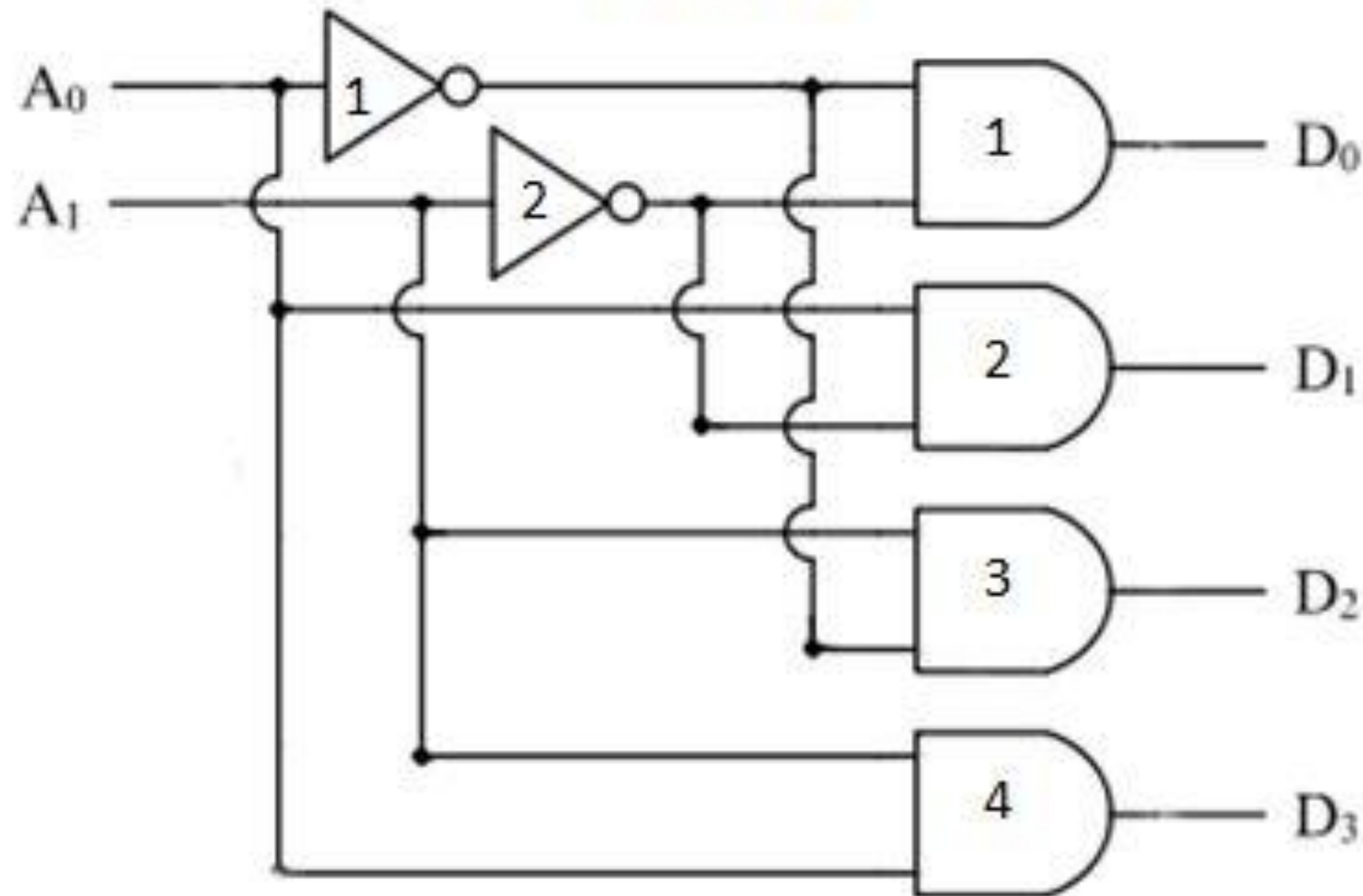

Truth Table

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Equations

$$D_0 = \bar{A}_1 \cdot \bar{A}_0$$


$$D_1 = \bar{A}_1 \cdot A_0$$

$$D_2 = A_1 \cdot \bar{A}_0$$

$$D_3 = A_1 \cdot A_0$$




DECODERS

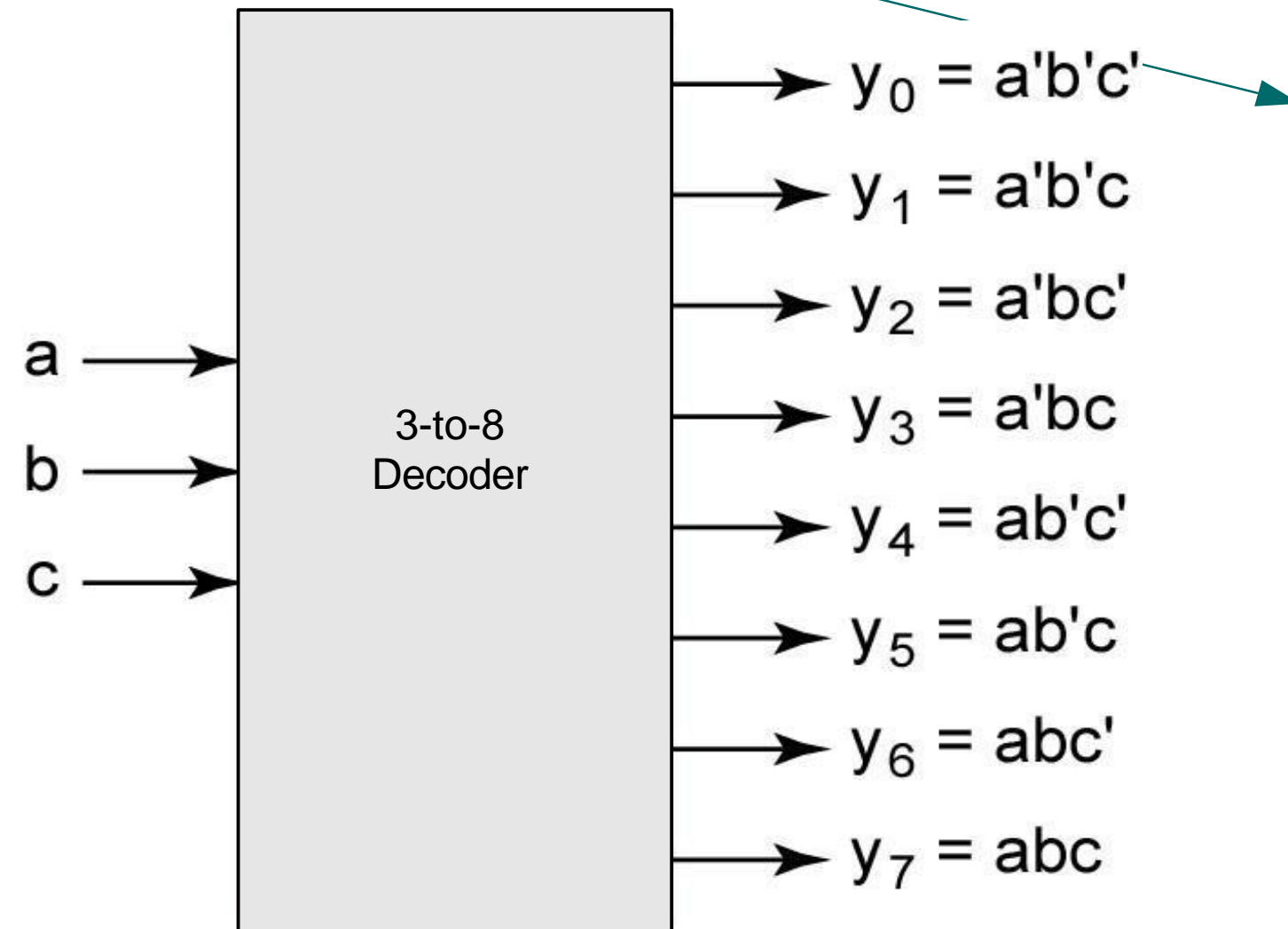

a	b	c	y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



Decoder with Enable

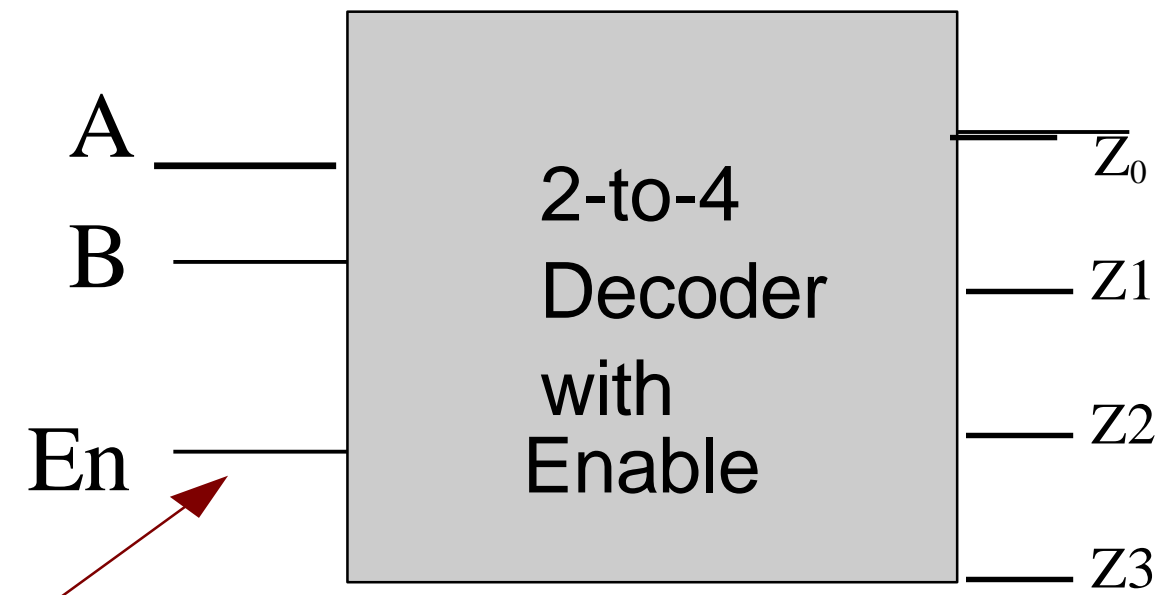

active-high enable


enabled

disabled

En	A	B	Z ₀	Z ₁	Z ₂	Z ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0



Decoder with Enable

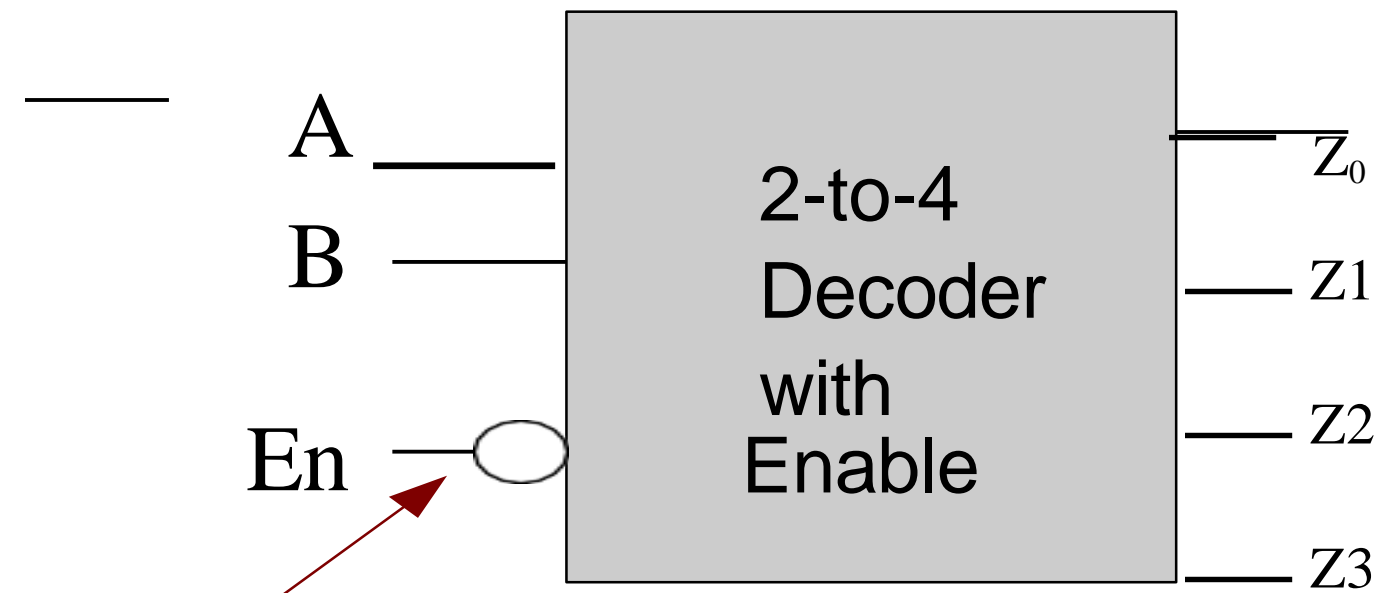

active-Low enable

enabled

disabled

En	A	B	Z ₀	Z ₁	Z ₂	Z ₃
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1
1	x	x	0	0	0	0



WHY ENCODERS?




An encoder has

- 2^n inputs
- n outputs

Outputs the binary value of the selected (or active) input.


Performs the inverse operation of a decoder. Issues

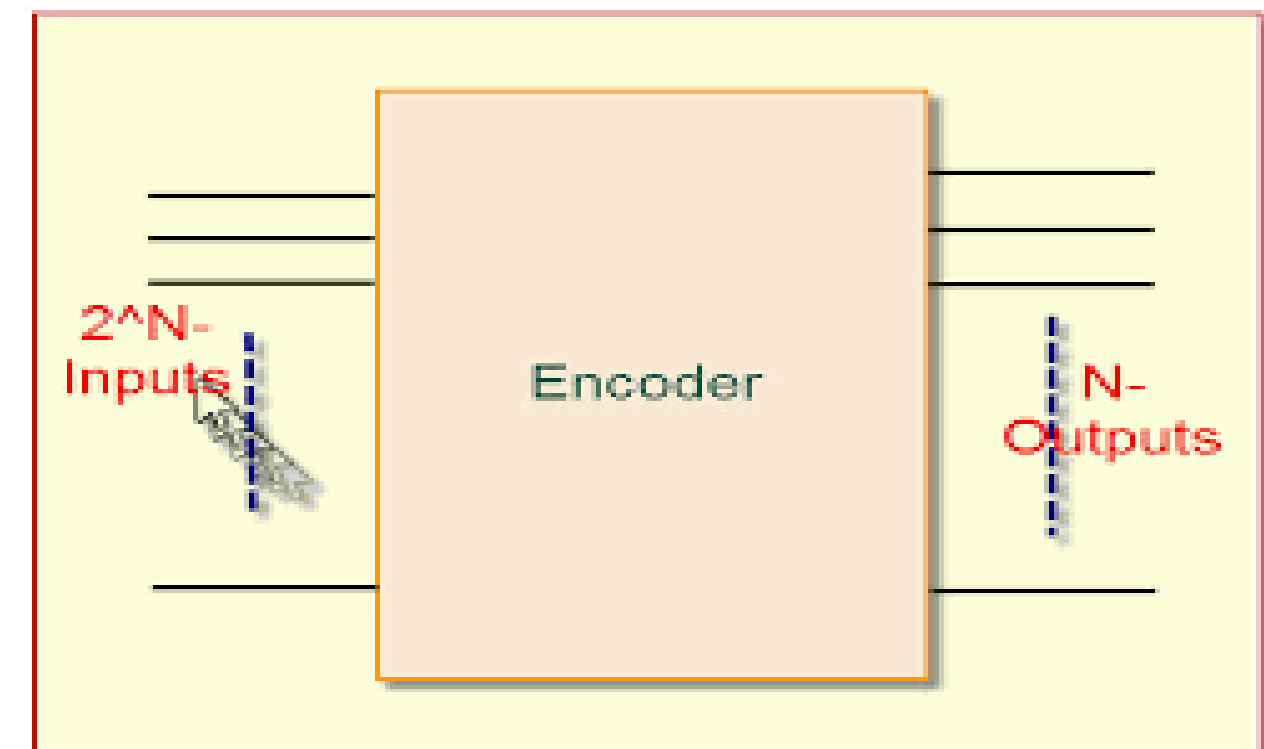- What if more than one input is active?
- What if no inputs are active?





Encoders

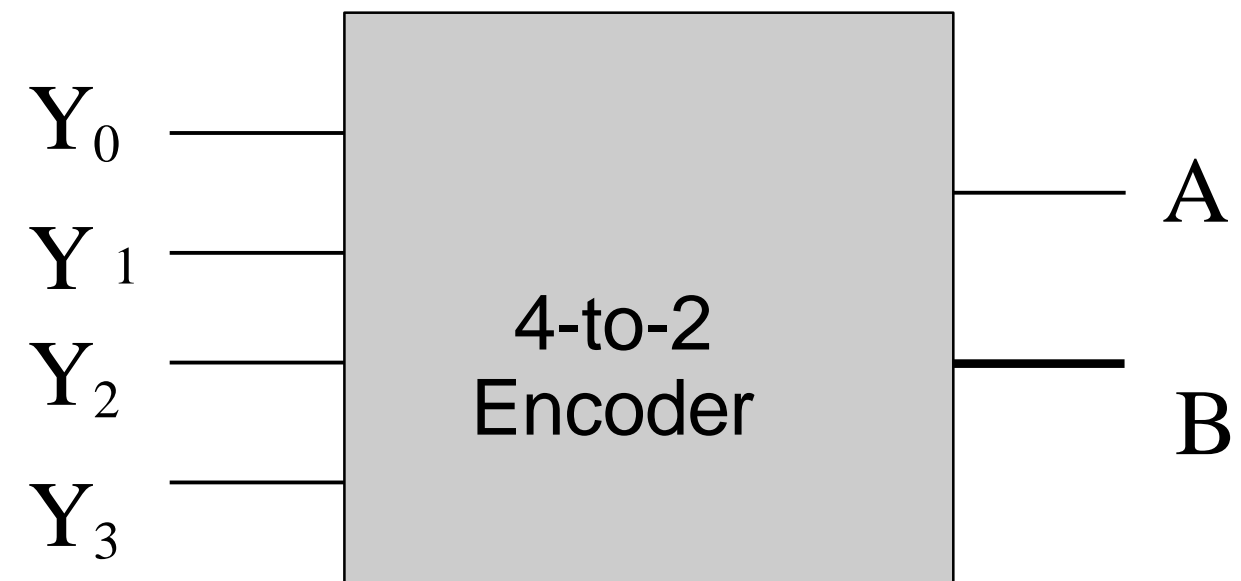

Y ₀	Y ₁	Y ₂	Y ₃	A	B
1	0	0 ₁₀	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1




Encoders



4 TO 2 LINE ENCODER

Logic diagram

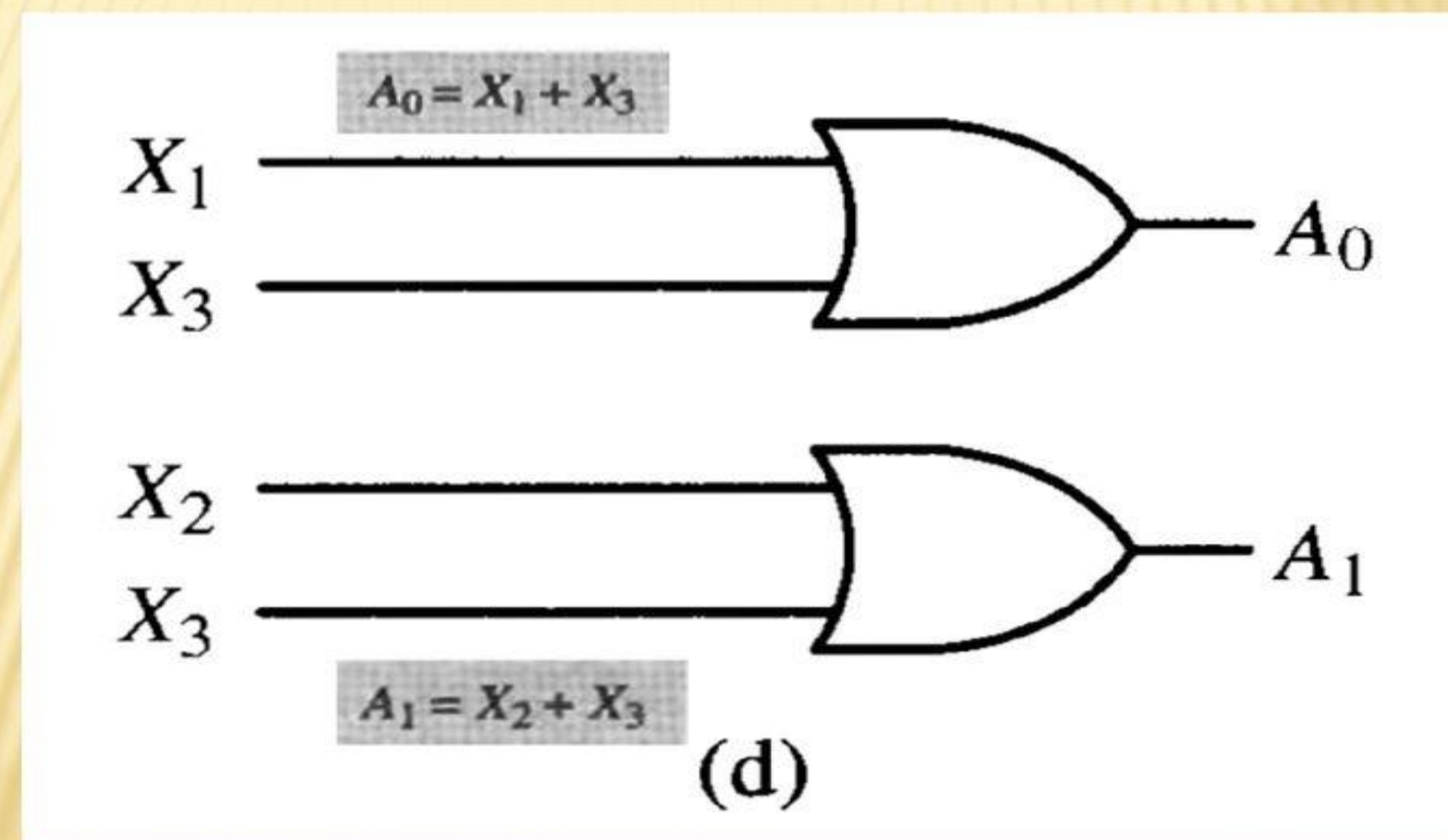



Priority Encoders




- If more than one input is active, the higher-order input has priority over the lower-order input.
 - The higher value is encoded on the output
- A valid indicator, d , is included to indicate whether or not the output is valid.
 - Output is invalid when no inputs are active
 - $d = 0$
 - Output is valid when at least one input is active
 - $d = 1$

12



Priority Encoders

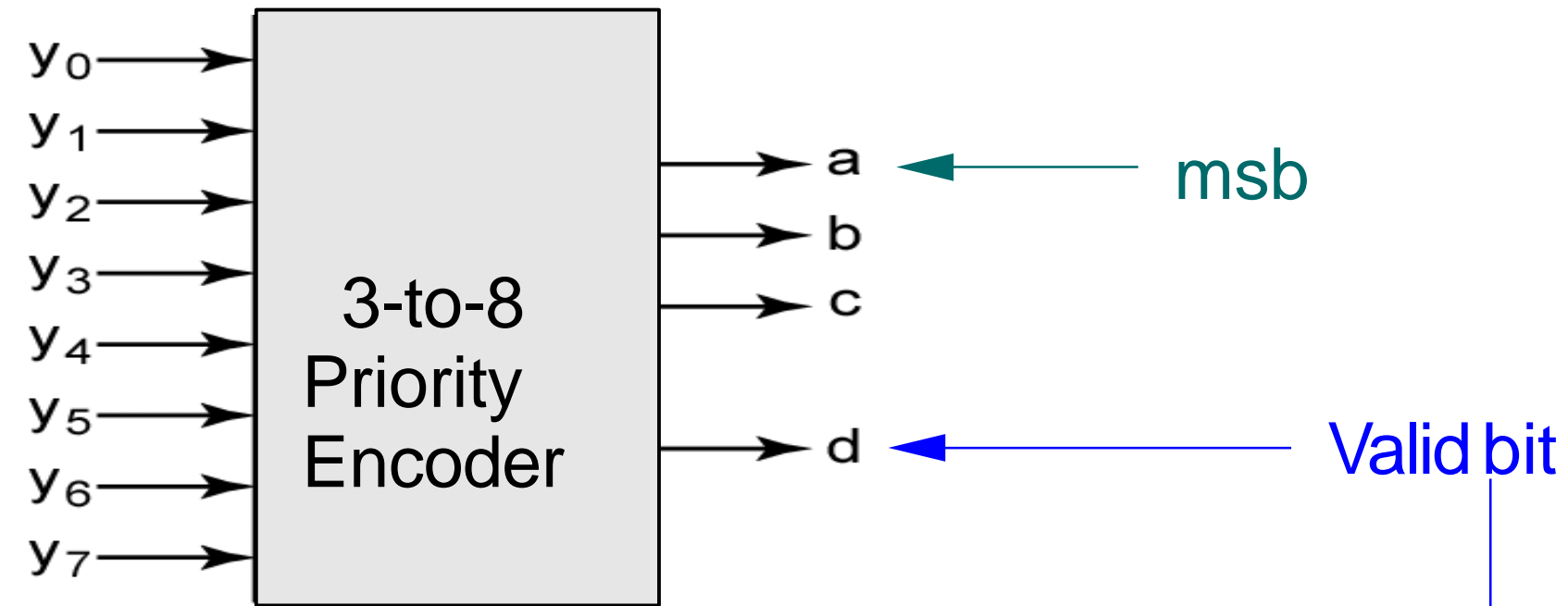

y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1



Using an n -output Decoder



- Use an n -output decoder to realize a logic circuit for a function with n minterms.
- Each minterm of the function can be mapped to an output of the decoder.
- For each row in the truth table, for the function, where the output is 1, sum (or “OR”) the corresponding outputs of the decoder.

14

- That is, for each minterm in the minterm expansion of the function, OR the corresponding outputs of the decoder.

Leave remaining outputs of the decoder unconnected.



Using an n -output Decoder



Example

- Using a 3-to-8 decoder, design a logic circuit to realize the following Boolean function
- $F(A,B,C) = \sum m(2, 3, 5, 6, 7)$



Using an n -output Decoder



Example

- Using a 2-to-2 decoder, design a logic circuit to realize the following Boolean function

16

$$F(A,B,C) = \sum m(0, 1, 4, 6, 7)$$



ASSESSMENT



1. What is a Encoder?
2. Device which converts an input device state into a binary representation of ones or zeros is termed as
 1. **Encoder**
 2. Decoder
 3. Multiplexer
 4. Data selector
3. A decoder converts n inputs to _____ outputs.(2^n)
4. ----- are building blocks of encoders.(Ans - OR gate)
5. Draw the block diagram of 2x4 decoder.

17



THANK YOU