



SNS COLLEGE OF TECHNOLOGY

(An Autonomous Institution)

COIMBATORE-35

Accredited by NBA-AICTE and Accredited by NAAC – UGC with A++ Grade

Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai



**23EET202 / DIGITAL ELECTRONICS AND LINEAR
INTEGRATED CIRCUITS**

II YEAR / III SEMESTER

**UNIT-III: DESIGN OF SEQUENTIAL CIRCUITS, PLD,
VHDL**

DESIGN OF SEQUENTIAL CIRCUITS



TOPIC OUTLINE

Sequential Circuits – Counters

Design Procedure

Example – 2/3/4 bit counter

Recap





SEQUENTIAL CIRCUITS: COUNTERS



- **Counters** are circuits that cycle through a specified number of states.
- **Two types of counters:**
 - ❖ synchronous (parallel) counters
 - ❖ asynchronous (ripple) counters
- **Ripple counters** allow some flip-flop outputs to be used as a source of clock for other flip-flops.
- **Parallel counters** apply the same clock to all flip-flops.





DESIGN - PROCEDURE




- Read the problem statement given. Draw the **state diagram** according to it
- Develop a **state table** if required
- Develop **excitation table** with the question asked flip flop (if not choose 'T' flip flop)
- Derive the **minimized expression** using K map (note: use present state as input to the flip flop)
- Realize with **logic gates and flip flops**
- Practically implement this circuit using **Logic ICs** and verify the result





Synchronous (Parallel) Counters

 - **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- We can design these counters using the sequential logic design procedure.
- **Example 1 :** Design a 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).



Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1




- 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J,K inputs).

Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$


$$TA_0 = 1$$

 




- Example 2:** Design a 3-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).


Present state			Next state			Flip-flop inputs		
A_2	A_1	A_0	A_2^+	A_1^+	A_0^+	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

$$TA_2 = A_1 \cdot A_0$$

 

$$TA_1 = A_0$$

 

$$TA_0 = 1$$




- 3-bit synchronous binary counter (cont'd).

$$TA_2 = A_1 \cdot A_0$$

$$TA_1 = A_0$$

$$TA_0 = 1$$

 



- Note that in a binary counter, the n^{th} bit (shown underlined) is always complemented whenever

$$\underline{0}11\dots11 \rightarrow \underline{1}00\dots00$$

$$\text{or } \underline{1}11\dots11 \rightarrow \underline{0}00\dots00$$

- Hence, X_n is complemented whenever

$$X_{n-1}X_{n-2} \dots X_1X_0 = 11\dots11.$$

- As a result, if T flip-flops are used, then

$$TX_n = X_{n-1} \cdot X_{n-2} \cdot \dots \cdot X_1 \cdot X_0$$





RECAP..



Thank You